

General System Architecture

- Both myip_v1_0.vhd and matrix_multiply.vhd are mealy FSMs.
 - Figure 2 and 3 shows "Moore-like" architecture. However, some values within each state depends on external values input values which makes it "Mealy".

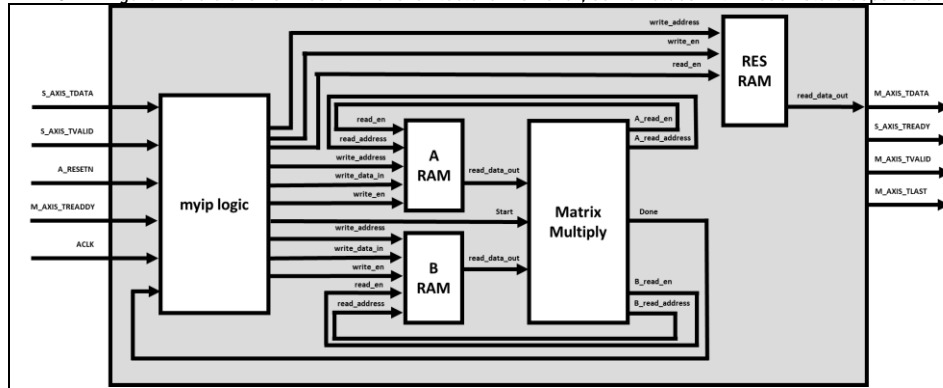


Figure 1: Generic System Architecture Derived From Synthesized Schematic

Summarised Explanation of System Architecture:

Our code utilises both sequential and combinational circuit, for a more detailed and elaborated look, please refer to the codes, comments are available for easier understanding.

Myip states: Idle, Read_Inputs, Compute, Write_Outputs, Write_Buffer [Figure 2. Depicts the FSM flow when planning the processes]

- Idle:**
- Registers are initialised as 0, when S_AXIS_TVALID = '1' state goes to Read_Inputs
- Read_Inputs:**
- myip reads data from the input memory file via S_AXIS_TDATA
 - These data is then written in A and B rams for matrix A and B respectively when A/B write_en is asserted in order when writing to their respective rams, a read_counter is utilised for tracking and allocation of memory. Once read_counter indicated that all elements of matrix A and B have been read and written into their respective rams, the states goes to compute
- Compute:**
- Start = '1' is asserted matrix_multiply coprocessor will then be utilised, one matrix_multiply has completed its processes, Done = '1' is asserted and state goes to Write_Output
- Write_Outputs and Write_Buffer:**
- Write_flag is utilised to toggle between Write_outputs and Write_buffer as 3 cycles is needed when delivering the outputs to result memory
 - Address is first updated for RES_read_address, M_AXIS_TDATA will then be updated with values from RES_read_data_out
 - Once the data is ready to be presented to result memory, M_AXIS_TVALID is then asserted to '1' and thus updating the result memory
 - write_counter is used to for address and progress tracking. Once write_counter tracks that all data has been present to the result memory, M_AXIS_TLAST is asserted to '1' and state goes back to Idle for reset.

Matrix_multiply state: Idle, Buff, Add, Reset [Figure 3. Depicts the FSM flow when planning the processes]

- Idle:**
- Registers initialised as 0, state goes to Buff
- Buff:**
- Buff here acts as a buffer for registers to be updated during the Counter increment and Product + Sum processes, state goes to Add
- Add:**
- Here (product) P is product of the desired value from matrix A and B, and it is Summed based on $Sum \leq Sum + P$. Note: ever other state P is 0 and Sum = Sum
 - Address counters for A and B are utilised to keep track and of the data being used and progress
 - Once B_address_counters reaches the last address in B ram, state goes to reset
- Reset:**
- Here Sum resets to 0, RES_address_counter tracks whether all the Summed values for the output has been allocated to the desired address
 - Once all the data has been sent to RES and the state goes back to Idle, else if not completed the cycle resets with B_address_counter being and state goes to Buff

Finite State Machines

 


Figure 2: my_ip FSM

Combinational Logic / signals outside of clock	
A_write_en	RES_read_address
B_write_en	M_AXIS_TDATA(7 downto 0)
RES_read_en	M_AXIS_TLAST
M_AXIS_TVALID	B_write_address

Table 1i: Combinational Logic at my_ip

 


Figure 3: matrix_multiply FSM

Combinational Logic / signals outside of clock	
Done	B_read_en
RES_write_en	P
A_read_en	RES_write_data_in

Table 2i: Combinational Logic at matrix_multiply

Non Combinational Logic / Signals within clock		Non Combinational Logic / Signals within clock	
• Start	• write_flag	• A_address_counter	• RES_address_counter
• Done	• A_write_data_in	• B_address_counter	• sum
• read_counter	• B_write_data_in		
• write_counter	• A_write_address		
• S_AXIS_TREADY			

Table Iii: Non-Combinational Logic at my_ip

Table Iii: Combinational Logic at matrix_multiply

Resource Usage					Resource Usage				
Site Type	Used	Fixed	Available	Util%	Site Type	Used	Fixed	Available	Util%
Slice LUTs*	166	0	53200	0.31	Slice LUTs*	168	0	53200	0.32
LUT as Logic	142	0	53200	0.27	LUT as Logic	144	0	53200	0.27
LUT as Memory	24	0	17400	0.14	LUT as Memory	24	0	17400	0.14
LUT as Distributed RAM	24	0			LUT as Distributed RAM	24	0		
LUT as Shift Register	0	0			LUT as Shift Register	0	0		
Slice Registers	117	0	106400	0.11	Slice Registers	79	0	106400	0.07
Register as Flip Flop	117	0	106400	0.11	Register as Flip Flop	79	0	106400	0.07
Register as Latch	0	0	106400	0.00	Register as Latch	0	0	106400	0.00
F7 Muxes	0	0	26600	0.00	F7 Muxes	0	0	26600	0.00
F8 Muxes	0	0	13300	0.00	F8 Muxes	0	0	13300	0.00

Figure 4: Before optimising

Figure 5: After optimising

Figure 4: Most of our values are within the clock process → not very efficient

Figure 5: We switch all the values we can to combinational to save as many registers as we can → gained 2 LUTs in exchange for a reduction of 38 registers.

○ Our "Combinational logic" is mostly behavioural and **without clock** → we declare the values out at every state

 


Figure 6: Post Synthesis Simulation (myip)



Figure 7: Post Synthesis Simulation (matrix_multiply)

Simulation @ myip:

- Idle: 1 clock cycle (cc), 100ns
- Read_Input: 13 cc, 1300ns
- Compute: 21 cc, 2100ns
- Write_Output+Write_Buffer: 8 cc, 800ns
- Total: 43 cycles, 4325ns (as per simulation result)